

GOAL- Designing a 555 astable vibrator circuit operating at about 500 Hz and about 50% duty cycle.


Designing- With respect to the 555 astable timer circuit diagram, it is required to find the values of resistors (R_a , R_b) and capacitors. The minimum value of resistor should be 1k ohm otherwise more amount of current would be in the discharge pin which is not advisable. Our kit has 1 microfarad and considering taking minimum no. of unique parts R_b has also been taken as 1k ohm.

➔ $F = 1.44 / (R_a + 2R_b) C$; $1.44 / (3000)10^{-6}$; $F \sim 500 \text{ Hz}$


➔ Duty Cycle = $1 - (R_b / (R_a + 2R_b))$; $\sim 67\%$

Below are the scope trace and measurements of NE555 timer:-

➤ **Scope Trace of NE555 timer**

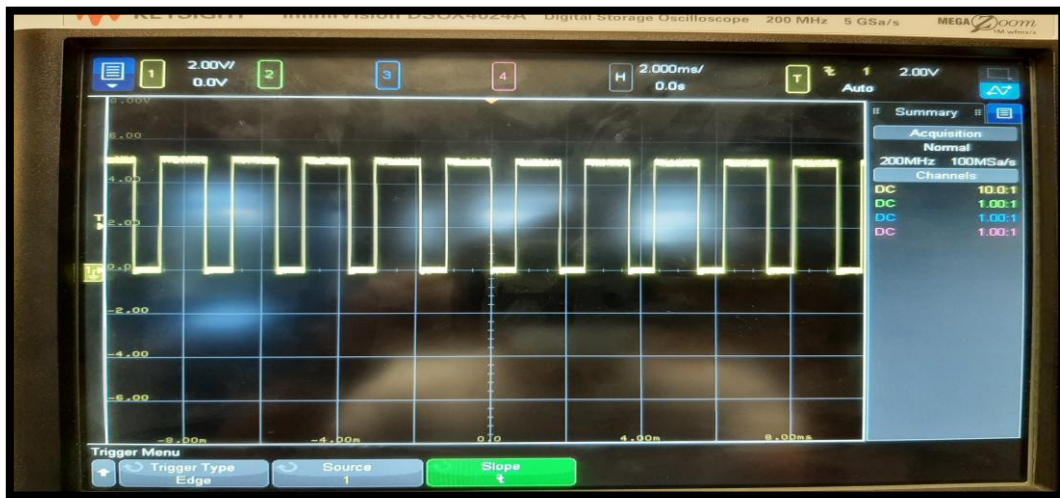

➤ **Rise and fall time of NE555 timer**

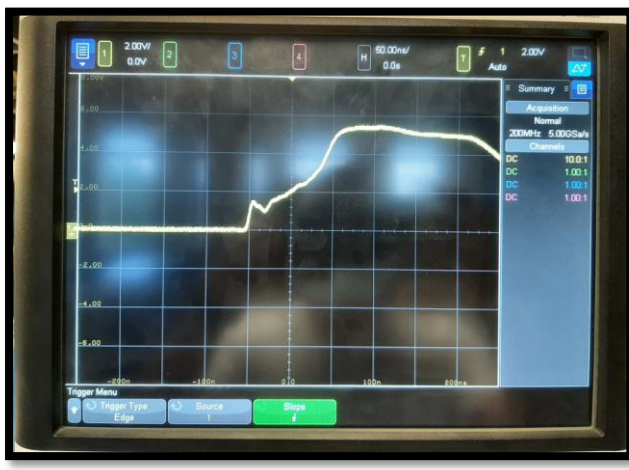

Figures of Merit

- ✓ Peak to peak voltage- 4.5 volts
- ✓ Frequency- 530.4 Hz
- ✓ Duty Cycle- 65.83%
- ✓ Rise Time- 115.620 ns (without load), 113.280 ns (with load)
- ✓ Fall time- 39.060 ns (without load), 38.280 ns (with load)

With respect to the datasheet the rising and falling time for NE555 timer is typically 100ns.

✓ Rise and fall time of 7555 Timer



Figures of Merit

- ✓ Peak to peak voltage- 5 volts
- ✓ Frequency- 530.4 Hz
- ✓ Duty Cycle- 63.57%
- ✓ Rise Time- 115.620 ns (without load), 113.280 ns (with load)
- ✓ Fall time- 39.060 ns (without load), 38.280 ns (with load)

With respect to the datasheet the rising and falling time for 7555 timer is typically 75ns.
